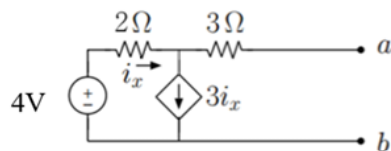



## Homework 3

Due: Wednesday March 12, 2025, 11:59 pm

1. In the following circuit find the open-circuit voltage and the short-circuit current between nodes a to b and determine the Thevenin and Norton equivalent of the network between nodes a and b.

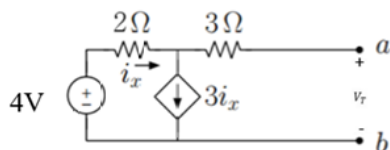**Solution:**

To find the open-circuit voltage, apply KCL at the upper node:




$$\frac{4 - V_T}{2} = 3i_x$$

$$\frac{4 - V_T}{2} = 3 \left( \frac{4 - V_T}{2} \right)$$

$$V_T = 4V$$

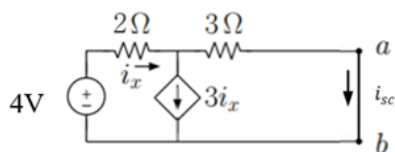To find the short circuit current, apply KVL at left inner loop:



$$4 = 2i_x + 3i_{sc}$$

Since  $i_x = -\frac{i_{sc}}{2}$ , the short circuit current is:


$$2 \left( -\frac{i_{sc}}{2} \right) + 3i_{sc} = 4$$

$$i_{sc} = 2A$$

To solve for  $R_T$ ,

$$R_T = \frac{V_T}{i_{sc}} = 2\Omega$$


Therefore, the Thevenin equivalent is:

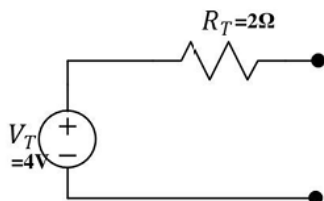

the Norton equivalent is:



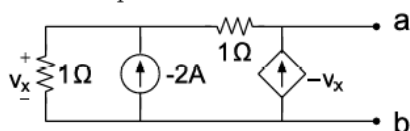2. Determine the Thevenin equivalent of the following network between nodes  $a$  and  $b$ , and then determine the available power of the network:



**Solution:**

To get the open-circuit voltage we analyze the circuit as shown in the problem statement. Applying KCL at the upper left node yields

$$-2 - v_x = v_x,$$

which gives

$$v_x = -1\text{V}.$$


Loop equation around the outer loop can be written as

$$v_x - v_x - v_{ab} = 0,$$

which gives

$$v_{oc} = v_{ab} = 0.$$

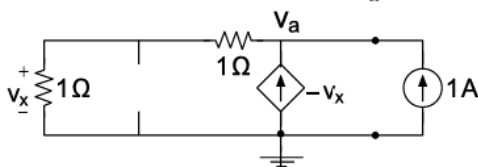Hence the Thevenin voltage is 0. It can be shown that the short-circuit current for the circuit is also 0. In this case we couldn't obtain the equivalent resistance by dividing  $v_{oc}$  by  $i_{sc}$ . To find  $R_{eq}$  we set the independent source to zero and add a test signal:



Writing the KCL equation for node  $v_a$ , we have

$$1 - v_x = v_x,$$

which gives

$$v_x = \frac{1}{2}\text{V}.$$


The same current flows through the two  $1\Omega$  resistors, which yields

$$v_a = 2v_x = 1\text{V}.$$

The equivalent resistance can thus be calculated as,

$$R_{eq} = \frac{v_a}{1\text{A}} = 1\Omega.$$


The Thevenin equivalent circuit is:

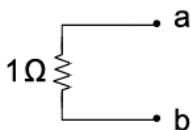

As a result, the available power is:

$$p_{av} = 0.$$


3. Consider the circuit below.

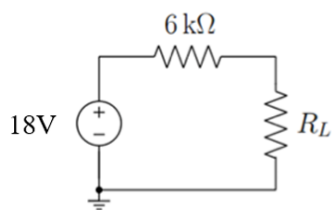

Calculate the absorbed power in  $R_L$  for

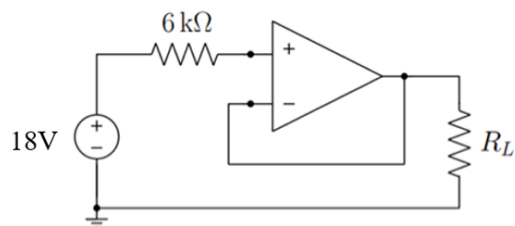
- (a)  $R_L = 3\text{ k}\Omega$
- (b)  $R_L = 6\text{ k}\Omega$
- (c)  $R_L = 12\text{ k}\Omega$

Next, consider the circuit below, which implements a buffer between the source and the load. Assume the circuit behaves linearly and make use of the ideal op-amp approximations.



Calculate the absorbed power in  $R_L$  for

- (d)  $R_L = 3\text{ k}\Omega$
- (e)  $R_L = 6\text{ k}\Omega$
- (f)  $R_L = 12\text{ k}\Omega$
- (g) Compare your answers from parts (a)-(c) to parts (d)-(f) and comment on why the power absorbed by the load is different for the two circuit designs (e.g., consider why one circuit delivers more power to the load and where that power comes from).

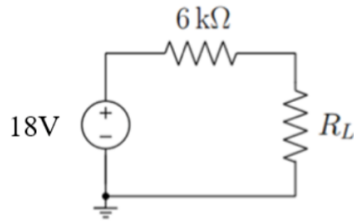**Solution:**

First, we can calculate the voltage across  $R_L$ .

$$V_L = 18 \frac{R_L}{6k + R_L}$$

Next, we can calculate the absorbed power in  $R_L$ .

$$P_L = \frac{V_L^2}{R_L} = 324 \frac{R_L}{(R_L + 6k)^2}$$

Therefore, the absorbed power is

$$(a) P_L = 0.012W$$

$$(b) P_L = 0.0135W$$

$$(c) P_L = 0.012W$$

Next, consider the circuit below, which implements a buffer between the source and the load. Assume the circuit behaves linearly and make use of the ideal op-amp approximations. Calculate the absorbed power in  $R_L$  for


$$(d) R_L = 3k\Omega$$

$$(e) R_L = 6k\Omega$$

$$(f) R_L = 12k\Omega$$

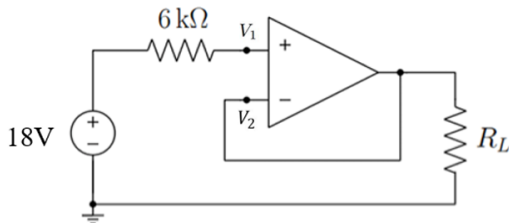**Solution:**

First, we need to calculate the voltage across  $R_L$ .



We will have a relationship between  $V_1$  and  $V_2$  which is:

$$V_1 = V_2 = 18V$$

With the voltage and resistance of the load, we can calculate the consumed energy.


$$P_L = \frac{V_2^2}{R_L}$$

$$(a) P_L = 0.108W$$

$$(b) P_L = 0.054W$$

$$(c) P_L = 0.027W$$

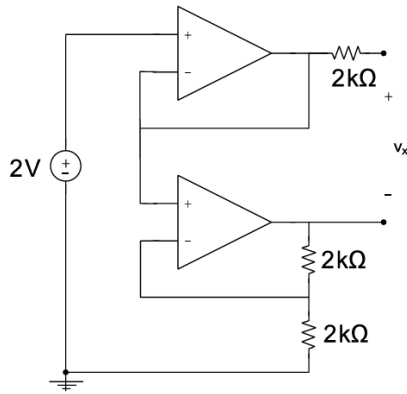4. In the op-amp circuit shown below, determine the voltage  $v_x$  assuming linear operation.



**Solution:**

Considering the ideal op-amp assumptions, we have  $v^+ = v^- = 2V$  for both op-amps. At the bottom of the circuit we identify a non-inverting amplifier with a gain of

$$G = 1 + \frac{2k\Omega}{2k\Omega} = 2,$$


with the output

$$v_{bottom} = G \times 2V = 4V.$$


At the top of the circuit we have a voltage follower and no current flowing through the resistor. Consequently, the output  $v_{top}$  is 2V. Finally we obtain

$$v_x = v_{top} - v_{bottom} = 2V - 4V = -2V.$$

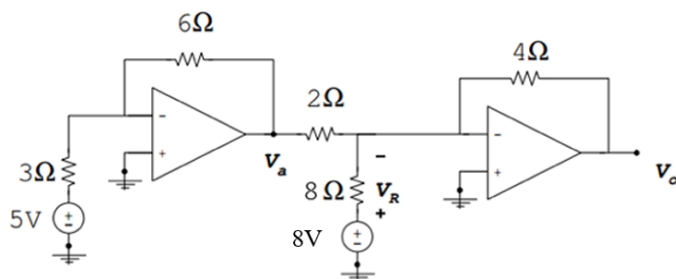5. In the op-amp circuit shown below, determine the voltages  $V_a$ ,  $V_R$ , and  $V_o$ . Assume the circuit behaves linearly and make use of the ideal op-amp approximation.



**Solution:**

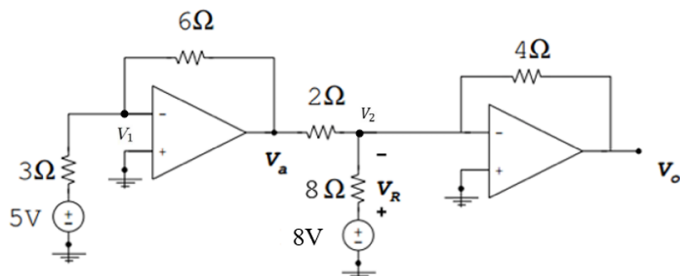

To find the  $V_a$ , apply KCL at node  $V_1$ :

$$\frac{5 - V_1}{3} + \frac{V_a - V_1}{6} = 0$$

According to the characteristics of op-amp,  $V_1$  becomes:

$$V_1 = 0V$$

Therefore, we can calculate  $V_a$ .

$$V_a = -10V$$

According to the characteristics of op-amp,  $V_2$  becomes:

$$V_2 = 0V$$

Therefore, we can calculate  $V_R$ .

$$V_R = 8 - V_2 = 8V$$

To find the  $V_o$ , apply KCL at node  $V_2$ :

$$\frac{V_a - V_2}{2} + \frac{V_R}{8} = \frac{V_2 - V_o}{4}$$

$$V_o = -\frac{4V_a + V_R}{2} = 16V$$