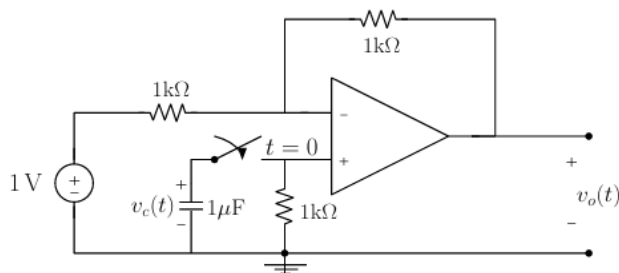


Homework 4

Due: Wednesday March 19, 2025, 11:59 pm

1. Assuming linear operation and making use of the ideal op-amp approximations, determine $v_o(t)$ at $t = 1$ ms in the following circuit. Consider $v_c(0) = -1$ V.

**Solution:**

Assuming linear operation there is no current flowing into the op-amp through either terminals (+) nor (-). So we can isolate the RC circuit with time constant $\tau = RC = (1\text{k}\Omega)(1\mu\text{F}) = 1\text{ms}$, which has the general solution:

$$v_c(t) = K_1 e^{-t/\tau} + K_2.$$

When $t \rightarrow \infty$ all the charge in the capacitor should be gone, therefore

$$v_c(t \rightarrow \infty) = 0 = K_2$$

Applying initial condition yields

$$v_c(0^+) = v_c(0^-) = -1\text{ V} = K_1 + K_2 \Rightarrow K_1 = -1\text{ V}.$$

Therefore $v_c(t)$ is

$$v_c(t) = -e^{-\frac{t}{1\text{ms}}} \text{ V},$$

for $t > 0$. Writing a KCL equation in the (-) terminal of the op-amp where $v_- \approx v_+ = v_c(t)$, we have

$$\frac{1\text{V} - v_c(t)}{1\text{k}\Omega} = \frac{v_c(t) - v_o(t)}{1\text{k}\Omega},$$


which simplifies to

$$\begin{aligned} v_o(t) &= 2v_c(t) - 1\text{ V} \\ &= -2e^{-\frac{t}{1\text{ms}}} - 1\text{ V}. \end{aligned}$$

Evaluating at $t = 1\text{ms}$,

$$\begin{aligned} v_o(t = 1\text{ms}) &= -2e^{-1} - 1\text{ V} \\ &\approx -2 * 0.37 - 1 = -1.74\text{ V}. \end{aligned}$$

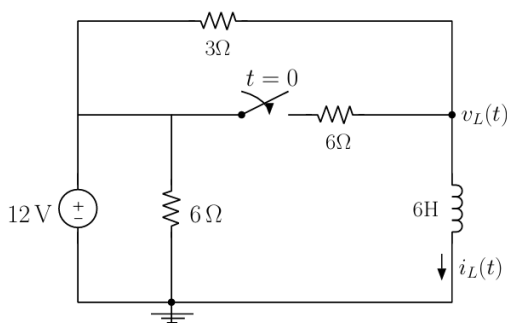2. The circuit shown below is in DC steady-state before the switch flips at $t = 0$. Find $v_L(0^-)$ and $i_L(0^-)$, as well as $i_L(t)$ and $v_L(t)$, for $t > 0$.




Solution:

In the DC steady-state, before closing the switch, the inductor acts like a short, then $v_L(0^-) = 0\text{V}$. Therefore by Ohm's Law we have the initial condition

$$i_L(0^-) = \frac{12\text{V}}{3\Omega} = 4\text{A}.$$

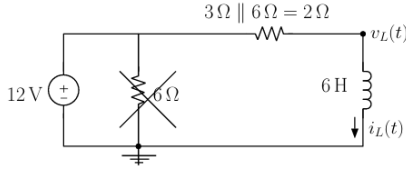After closing the switch we have the following circuit



In this case we neglected the 6Ω resistance, since it is in parallel with a voltage source. The general solution for the current in the inductor in an RL circuit with time constant $\tau = L/R = (6\text{H})/(2\Omega) = 3\text{s}$ is

$$i_L(t) = K_1 e^{-t/\tau} + K_2.$$

When $t \rightarrow \infty$ the inductor acts like a short, therefore, by Ohm's Law

$$i_L(t \rightarrow \infty) = \frac{12\text{V}}{2\Omega} = 6\text{A} = K_2$$

Applying the initial condition yields

$$i_L(0^+) = i_L(0^-) = 4\text{A} = K_1 + K_2 \Rightarrow K_1 = -2\text{A}.$$

Therefore $i_L(t)$ is


$$i_L(t) = 6 - 2e^{-\frac{t}{3\text{s}}}\text{A},$$

for $t > 0$.

Using the $v - i$ relation for the inductor $v_L = L \frac{d}{dt} i(t)$, we obtain

$$\begin{aligned} v_L(t) &= 6\text{H} \times \frac{d}{dt} (6 - 2e^{-\frac{t}{3}})\text{A} \\ &= 6\text{V} \times \left(\frac{2}{3}e^{-\frac{t}{3}}\right) \\ &= 4e^{-\frac{t}{3}}\text{V}. \end{aligned}$$

3. Assume the switch has been in position A for a long time. It moves to position B at time $t = 0\text{s}$, and back to position A at time $t = 2\text{s}$. Find values L and R such that $i(t) = 1 - e^{-1}\text{A}$ at $t = 2\text{s}$, and $i(t) = (1 - e^{-1})e^{-1}\text{A}$ at $t = 6\text{s}$.

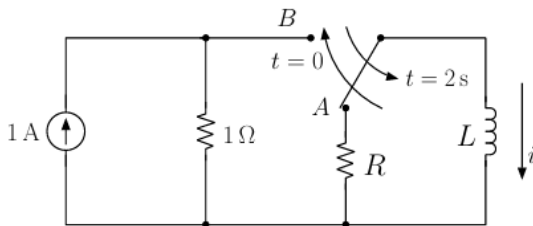**Solution:**

Before $t = 0$, the circuit is in steady-state and without any sources there is no current flowing through the inductor, i.e.

$$i(0^-) = i(0^+) = 0\text{A}.$$

After the switch moves to position B we have an RL circuit with time constant $\tau = L/(1\Omega)$ and general equation for the current through the inductor

$$i(t) = K_1 e^{-t/\tau} + K_2.$$

If the switch would stay in position B for a long time, the inductor would become a short and the current flowing through it would be 1 A, which means

$$K_2 = 1 \text{ A.}$$

Applying the initial condition we obtain K_1 :

$$i(0^-) = i(0^+) = 0 \text{ A} = K_1 + K_2 \Rightarrow K_1 = -1 \text{ A.}$$

Therefore the current through the inductor in the interval $0 < t < 2 \text{ s}$ is

$$i(t) = 1 - e^{-t/L}.$$

When the switch moves back to position A at $t = 2 \text{ s}$, the current through the inductor remains

$$i(2^+) = i(2^-) = 1 - e^{-2/L} \text{ A.}$$

Now the general equation for the current has a new time constant: $\tau = L/R$ and starting at $t = 2 \text{ s}$ is

$$i(t) = K_3 e^{-(t-2)/\tau} + K_4.$$

With no source in the new circuit we have $i(t \rightarrow \infty) = 0$ and consequently $K_4 = 0 \text{ A}$. Applying the initial condition we can obtain K_3 :

$$i(2^+) = i(2^-) = 1 - e^{-2/L} \text{ A} = K_3 e^{-(2-2)/\tau} \Rightarrow K_3 = 1 - e^{-2/L} \text{ A.}$$

Hence the equation for the current through the inductor for $t > 2 \text{ s}$ is

$$i(t) = \left(1 - e^{-2/L}\right) e^{-\frac{(t-2)}{L/R}}.$$

The condition of the problem says that $i(t) = 1 - e^{-1} \text{ A}$ at $t = 2 \text{ s}$. Therefore, the inductor should be

$$L = 2 \text{ H.}$$


The second conditions tells us $i(t) = (1 - e^{-1}) e^{-1} \text{ A}$ at $t = 6 \text{ s}$, which means

$$-\frac{(t-2)}{L/R} \bigg|_{t=6 \text{ s}} = -1.$$

For this to be true, the resistor R should be

$$R = \frac{L}{4} = \frac{2}{4} = 0.5 \Omega$$

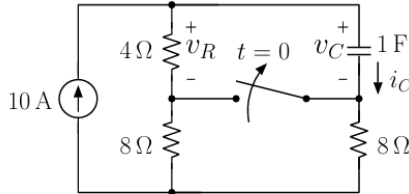4. Assume that the switch has been closed for a long time and it opens at $t = 0 \text{ s}$. Find and sketch $v_R(t)$, $v_C(t)$, and $i_C(t)$.



Solution:

In the steady-state, before the switch opens, i.e. $t < 0$, there is no current flowing through the fully charged capacitor

$$i_C(0^-) = 0.$$

And the voltage right before $t = 0$ can be obtained from Ohm's Law

$$v_R(0^-) = v_C(0^-) = v_C(0^+) = (10 \text{ A})(4 \Omega) = 40 \text{ V.}$$

After the switch opens, we notice that the Thevenin resistor that the capacitor sees between its terminals is

$$R_T = 4 + 8 + 8 = 20 \Omega.$$

And the general equation for the RC circuit with time constant $\tau = RC = 20$ s becomes

$$v_C(t) = K_1 e^{-t/20} + K_2.$$

When $t \rightarrow \infty$, there will be no current flowing through the capacitor, and it will be fully charged with the same voltage across the resistors in series 4Ω and 8Ω

$$v_C(t \rightarrow \infty) = (10 \text{ A}) (4 \Omega + 8 \Omega) = 120 \text{ V},$$

which yields

$$K_2 = 120 \text{ V}.$$

Finally applying the initial condition

$$v_C(0^+) = 40 \text{ V} = K_1 + K_2,$$

we obtain

$$K_1 = -80 \text{ V}.$$

Consequently the equation $v_C(t)$ for $t > 0$ becomes

$$v_C(t) = 120 - 80e^{-t/20} \text{ V}.$$

We can find $i_C(t)$ using the $v - i$ relation

$$i_C(t) = C \frac{dv_C}{dt} = 4e^{-t/20} \text{ A}.$$

From a KCL in the top node we can obtain

$$\frac{v_R(t)}{4 \Omega} + i_C(t) = 10 \text{ A},$$

which yields the voltage across the resistor

$$v_R(t) = 40 - 4i_C(t) = 40 - 16e^{-t/20} \text{ V}.$$

For sketching $v_R(t)$, $v_C(t)$, and $i_C(t)$, is useful to know some approximations of e^{-x} , e.g. $e^{-1} \approx 0.37$, and $e^{-5} \approx 0.01$, which has the following practical implications:

- After one time constant (τ), a capacitor has either discharged down to 37% of its initial charge (when discharging) or has reached 63% of its final charge (when charging).
- At five times the time constant (5τ) a capacitor is either almost fully charged (when charging) or almost completely discharged (when discharging).

