ECE 210 Homework

Homework 5

Due: Wednesday March 26, 2025, 11:59 pm

1. Consider the following circuit with $v(0^-) = 1V$. For t > 0, obtain:

$$\cos (4t) V \stackrel{+}{\underbrace{}} \underbrace{\frac{1}{16}}^{4\sqrt{3}} \Omega$$

- (a) the zero-state voltage across the capacitor's terminals, $v_{\rm ZS}(t)$,
- (b) the zero-input voltage across the capacitor's terminals, $v_{\rm ZI}(t)$,
- (c) the transient voltage across the capacitor's terminals, $v_{\rm tr}(t)$,
- (d) the steady state voltage across the capacitor's terminals, $v_{ss}(t)$, and
- (e) the total voltage across the capacitor's terminals, v(t).

Solution:

First we are going to find the ODE that rules the circuit. Applying KVL gives

$$\cos(4t) = v + v_R = v + R \times C \frac{dv}{dt}$$

which yields to the following ODE:

$$\cos(4t) = v + \frac{4\sqrt{3}}{16} \times \frac{dv}{dt},.$$

To solve this ODE we start from the particular solution

$$v_p(t) = A\cos(4t) + B\sin(4t).$$

Taking the derivative yields

$$\frac{dv_p(t)}{dt} = -4A\sin(4t) + 4B\cos(4t).$$

Substituting v(t) and $\frac{dv(t)}{dt}$ into the ODE, we obtain

$$\cos(4t) = A\cos(4t) + B\sin(4t) + \frac{\sqrt{3}}{4} \times [-4A\sin(4t) + 4B\cos(4t)]$$

This identity imposes the two constraints

$$A + B\sqrt{3} = 1$$
 and $B - A\sqrt{3} = 0$,

yielding

$$A = \frac{1}{4}$$
 and $B = \frac{\sqrt{3}}{4}$.

Therefore, the particular solution is

$$v_p(t) = \frac{1}{4}\cos(4t) + \frac{\sqrt{3}}{4}\sin(4t) V.$$

The homogeneous solution for the RC circuit has the form $v_h(t) = K_1 e^{-t/\tau}$, with $\tau = RC = \frac{\sqrt{3}}{4}$ s. Adding the homogeneous and the particular solutions yields to the general solution:

$$v(t) = v_h(t) + v_p(t) = K_1 e^{-t/\tau} + \frac{1}{4}\cos(4t) + \frac{\sqrt{3}}{4}\sin(4t) \text{ V}.$$

ECE 210 Homework

(a) From the general solution we can calculate the zero-state response, i.e. the solution that satisfies $v(0^-) = 0$:

$$0 = K_1 + \frac{1}{4} \Rightarrow K_1 = -\frac{1}{4}.$$

Therefore the zero-state solution is

$$v_{\rm ZS}(t) = -\frac{1}{4}e^{-\frac{4t}{\sqrt{3}}} + \frac{1}{4}\cos(4t) + \frac{\sqrt{3}}{4}\sin(4t) \text{ V}.$$

(b) The zero-input response can be obtained applying the initial condition to the homogeneous solution, i.e.

$$v_h(0^-) = 1 V = K_1 e^0 \Rightarrow K_1 = 1 V.$$

Therefore the zero-input response is

$$v_{ZI}(t) = e^{-\frac{4t}{\sqrt{3}}} \,\mathrm{V}.$$

(c) From the total response we notice that the transient response is

$$v_{\rm tr}(t) = \frac{3}{4}e^{-\frac{4t}{\sqrt{3}}} \, V,$$

(d) since that is the component of v(t) that vanishes as $t \to \infty$. The remainder is the steady state response, i.e.

$$v_{\rm ss}(t) = \frac{1}{4}\cos(4t) + \frac{\sqrt{3}}{4}\sin(4t) \text{ V}.$$

(e) The total voltage across the capacitor is the sum of the zero-input and the zero-state responses. Also, it is the sum of transient response and steady state response:

$$v(t) = v_{\rm ZI}(t) + v_{\rm ZS}(t) = v_{tr}(t) + v_{\rm ss}(t) = \frac{3}{4}e^{-\frac{4t}{\sqrt{3}}} + \frac{1}{4}\cos(4t) + \frac{\sqrt{3}}{4}\sin(4t) \text{ V}.$$

2. A second-order linear system is described by

$$\frac{d^2v}{dt^2} + 3\frac{dv}{dt} + 2v(t) = \cos(2t).$$

Confirm that the transient function

$$v_h(t) = Ae^{-t} + Be^{-2t}$$

is homogeneous solution of the ODE and that its particular solution can be expressed as

$$v_n(t) = H\cos(2t + \theta).$$

Determine the values of H and θ . Hint: See Example 3.20 in Section 3.4.3 of the textbook.

Solution:

Substitute the transient function into the linear system.

$$\frac{d^2v_h}{dt^2} + 3\frac{dv_h}{dt} + 2v_h(t) = Ae^{-t} + 4Be^{-2t} - 3Ae^{-t} - 6Be^{-2t} + 2Ae^{-t} + 2Be^{-2t} = 0$$

Thus it is a homogeneous solution of the ODE.

We then substitute $v_p(t)$ to the left hand side of the linear system.

$$\frac{d^{2}v_{p}}{dt^{2}} + 3\frac{dv_{p}}{dt} + 2v_{p}(t) = -4H\cos(2t+\theta) - 6H\sin(2t+\theta) + 2H\cos(2t+\theta)
= -2H\cos(2t+\theta) - 6H\sin(2t+\theta)
= -H(e^{j(2t+\theta)} + e^{-j(2t+\theta)}) + j3H(e^{j(2t+\theta)} - e^{-j(2t+\theta)})
= (-H+j3H)e^{j(2t+\theta)} + (-H-j3H)e^{-j(2t+\theta)}$$

ECE 210

Note that Eq. should be equal to

$$\cos(2t) = \frac{1}{2}(e^{j2t} + e^{-j2t}),$$

which leads to

$$(-H + j3H)e^{j\theta} = \frac{1}{2},$$
 $(-H - j3H)e^{-j\theta} = \frac{1}{2}$

We then have

$$\sqrt{(-H)^2 + (3H)^2} = \frac{1}{2}$$

Thus,

$$H = \frac{1}{2\sqrt{10}}.$$

$$\theta = -\left(\pi + \arctan\left(\frac{3H}{-H}\right)\right) = \arctan(3) - \pi.$$

3. Determine the phasor F of the following co-sinusoidal functions f(t):

- (a) $f(t) = -\sqrt{3}\cos(3t \frac{\pi}{6}),$
- (b) $f(t) = 4\sin(4t \frac{\pi}{2})$.

Solution:

- (a) $f(t) = -\sqrt{3}\cos(3t \frac{\pi}{6}) = \sqrt{3}\cos\left(3t + \pi \frac{\pi}{6}\right) = \sqrt{3}\cos\left(3t + \frac{5\pi}{6}\right)$. The magnitude of the cosine signal is $|F| = \sqrt{3}$. The phase shift is $\angle F = \frac{5\pi}{6}$ rad. Therefore the phasor is: $F = \sqrt{3}e^{j\frac{5\pi}{6}} = \sqrt{3}\angle 150^{o}$.
- (b) $f(t) = 4\sin(4t \frac{\pi}{2}) = 4\cos\left(\sqrt{3}t \frac{\pi}{2} \frac{\pi}{2} + 2\pi\right)$. In this case |F| = 4, $\angle F = \pi$ rad. Therefore the corresponding phasor is: $F = 4e^{j\pi} = 4\angle 180^o$.

4. Determine the phasor F of the following co-sinusoidal functions f(t):

- (a) $f(t) = 2\cos(2t + \frac{\pi}{3})$
- (b) $f(t) = A\sin(\omega t)$
- (c) $f(t) = -5\sin(\pi t)$

Solution:

- (a) $|f(t)| = 2, \angle f(t) = \frac{\pi}{3}$. So $F = 2 \angle \frac{\pi}{3}$.
- (b) $f(t) = A\cos\left(\omega t \frac{\pi}{2}\right)$. So $F = A\angle \frac{\pi}{2}$.
- (c) $f(t) = 5\cos\left(\pi t + \frac{\pi}{2}\right)$. So $F = 5 \angle \frac{\pi}{2}$.

5. Use the phasor method to express the following signals f(t) as single cosines:

- (a) $f(t) = 3\cos(4t) 4\sin(4t)$.
- (b) $f(t) = 3\cos(3t) + 3\cos(3t \pi/2)$.

ECE 210 Homework

Solution:

(a) $f(t) = -4\sin(4t) + 3\cos(4t) = 4\cos(4t + \frac{\pi}{2}) + 3\cos(4t)$. In phasor form $F = 4e^{+j\frac{\pi}{2}} + 3 = j4 + 3 = 5e^{j(\arctan(\frac{4}{3}))}$, which yields the time-domain form:

$$f(t) = 5\cos\left(4t + \arctan\left(\frac{4}{3}\right)\right) \approx 5\cos\left(4t + 0.9273\right),$$

with amplitude 5 and phase shift $\arctan\left(\frac{4}{3}\right) \approx 0.9273 \, \text{rad} = 53.1301^{\circ}$.

(b) $g(t) = 3\cos(3t) + 3\cos(3t - \pi/2)$. In phasor form $F = 3e^{-j\frac{\pi}{2}} + 3 = -j3 + 3 = 3\sqrt{2}e^{-j\frac{\pi}{4}}$, which yields

$$f(t) = 3\sqrt{2}\cos\left(3t - \frac{\pi}{4}\right),\,$$

with amplitude $3\sqrt{2}$ and phase shift $-\frac{\pi}{4}$ rad.